

# LOGICAL INTERFACE FOR USE WITH AUDIO CASSETTE TAPE RECORDER.

MARK WILSON.

3/10/79.



Fuses:

Conductors: 4635

Resistors: 3913


3915

Firing Data.

Peak temp + 850°C.

S-peak Molds: 186

Print thickness.

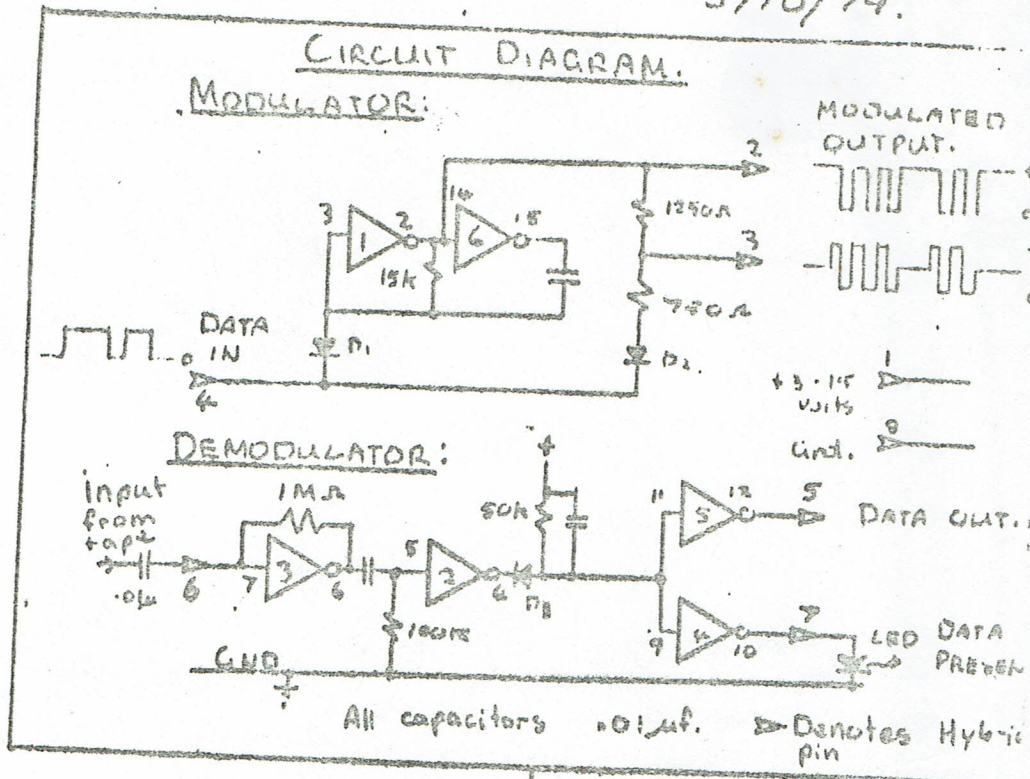


	Dried	Fired
Res. .01	27μ	18μm.
.02	26μ	24μm.
Cond. .02	32μ	16μ
.01		17μ
.06	33μ	23μ

### Values.

Target	Measured.		
	1	2	3
750	621	669	624
1250	1107	1106	1105
15k	21.8k	21.8k	22.6k
100k	107k	113k	101k
1M.	1.94M	1.7M	2.1M

### COMPONENT LAYOUT.

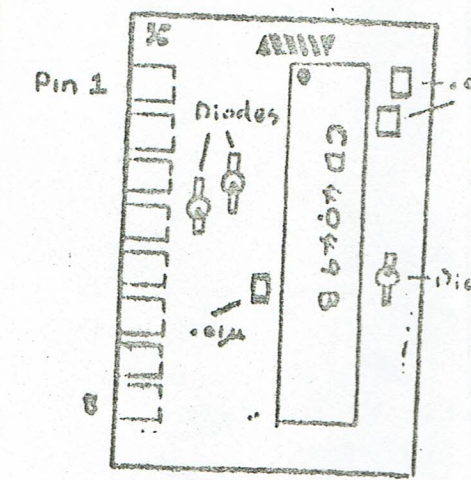


### ADD ON COMPONENTS.

- 1 x CD4049B HEX INVERTER.
  - 2 x .01μF Vitramon capacitors
  - 3 x MMD 6050 Diodes ML241.
  - 8 x DIL. Pins.
- Approximate cost. \$3.00
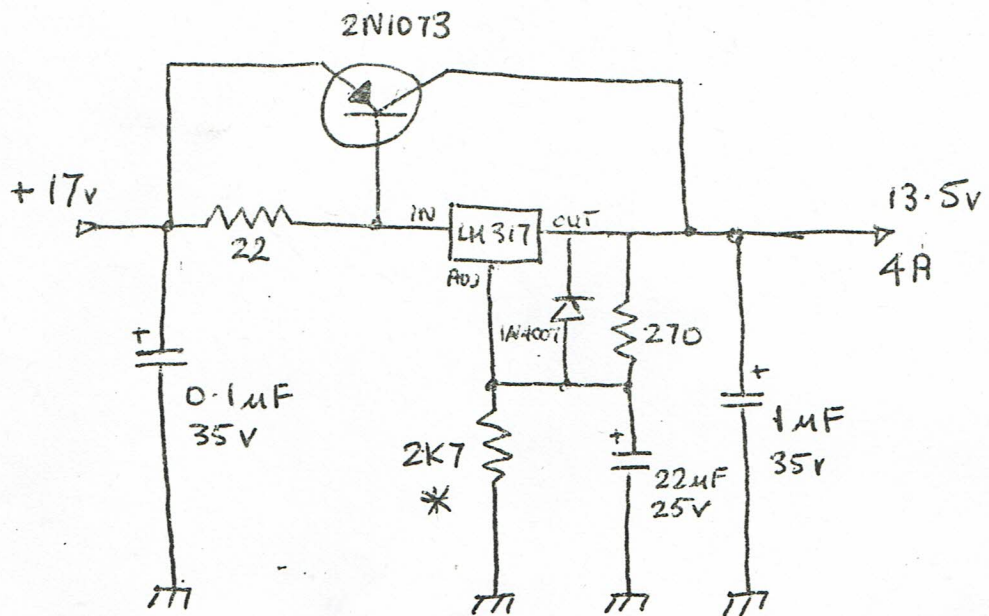
### CIRCUIT DESCRIPTION.

**MODULATOR:** This is formed from a simple 2 inverter oscillator which is turned on and off by the incoming data. Its on frequency is approx 2 kHz. D<sub>2</sub> holds the output at ~2.5 volts when the input is low.

**DEMODULATOR:** Inverter 3 acts as an amplifier. Its output is high pass filtered and squared up by Inu. 2. D<sub>3</sub> and its associated resistor and capacitor act as a leaky diode pump demodulator. Inverter 4 and 5 buffer the output. Both outputs are identical. One can be used



\* VALUE MAY BE CHANGED  
 UPTO 5K TO VARY O/P  
 VOLTS.

DC REGULATOR 4 AMP  
 1.5 - 30V OUTPUT